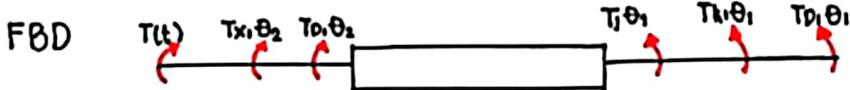


Problem No. 1



$$T(t) = T_j\theta_1 + T_{D1}\theta_1 + T_{k1}\theta_1 - T_{D1}\theta_2 - T_{k1}\theta_2$$


$$T(t) = j\ddot{\theta}_1 + D_1\dot{\theta}_1 + k\theta_1 - D_1\theta_2 - k\theta_2$$

$$\{ T(t) = \ddot{\theta}_1 + \dot{\theta}_1 + \theta_1 - \dot{\theta}_2 - \dot{\theta}_1 \}$$

$$T(s) = s^2\theta_1(s) + s\theta_1(s) + \theta_1(s) - s(\theta_2)(1) - \theta_2(s)$$

$$T(s) = \underset{A}{\theta_1(s)} [G^2(s+1)] - \theta_2(1)[s+1] \quad ①$$

FBD 2

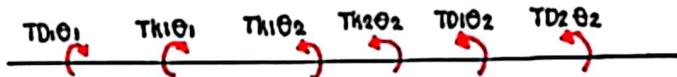

$$0 = T_{D1}\theta_2 + T_{D2}\theta_2 + T_{k1}\theta_2 + T_{k2}\theta_2 + T_{k2}\theta_2 - T_{D1}\theta_1 - T_{k1}\theta_1$$

$$0 = D_1\dot{\theta}_2 + D_2\dot{\theta}_2 + k_1\theta_2 + k_2\dot{\theta}_2 - D_1\dot{\theta}_1 - k_1\theta_1$$

$$\{ 0 = 2\theta_2 + 2\dot{\theta}_2 - \dot{\theta}_1 - \theta_1 \}$$

$$0 = 2s\theta_2(s) + 2(\theta_2)(s) - s\theta_1(s) - \theta_1(s)$$


$$0 = 2\theta_2(s)[s+1] - \theta_1(s)[s+1] \quad ②$$

$$\theta_2(s) = \frac{\begin{bmatrix} s^2+s+1 & T(s) \\ -(s+1) & 0 \end{bmatrix} - \frac{0 - [-T(s)(s+1)]}{2(s+1)(s^2+1)-(s+1)^2}}{\begin{bmatrix} (s^2+s+1) & -(s+1) \\ -(s+1) & 2(s+1) \end{bmatrix}}$$

$$= \frac{T(s)(s+1)}{(s+1)[2(s^2+s+1)-(s+1)]}$$


$$\theta_2(s) = \frac{T(s)}{2s^2+s+1}$$

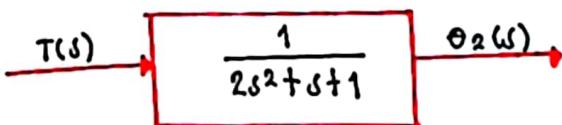
$$\frac{\theta_2(s)}{T(s)} = \frac{1}{2s^2+s+1}$$




$$\theta_1(s) = \frac{\begin{bmatrix} T(s) & -(s+1) \\ 0 & 2(s+1) \end{bmatrix} - \frac{2(s+1)+s}{2s^2+s+1}}{\begin{bmatrix} s^2+s+1 & -s+1 \\ -(s+1) & 2(s+1) \end{bmatrix}}$$

$$\frac{\theta_1(s)}{T(s)} = \frac{2(s+1)}{2s^2+s+1}$$

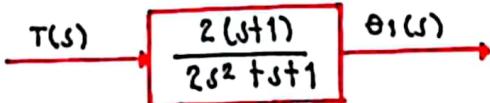

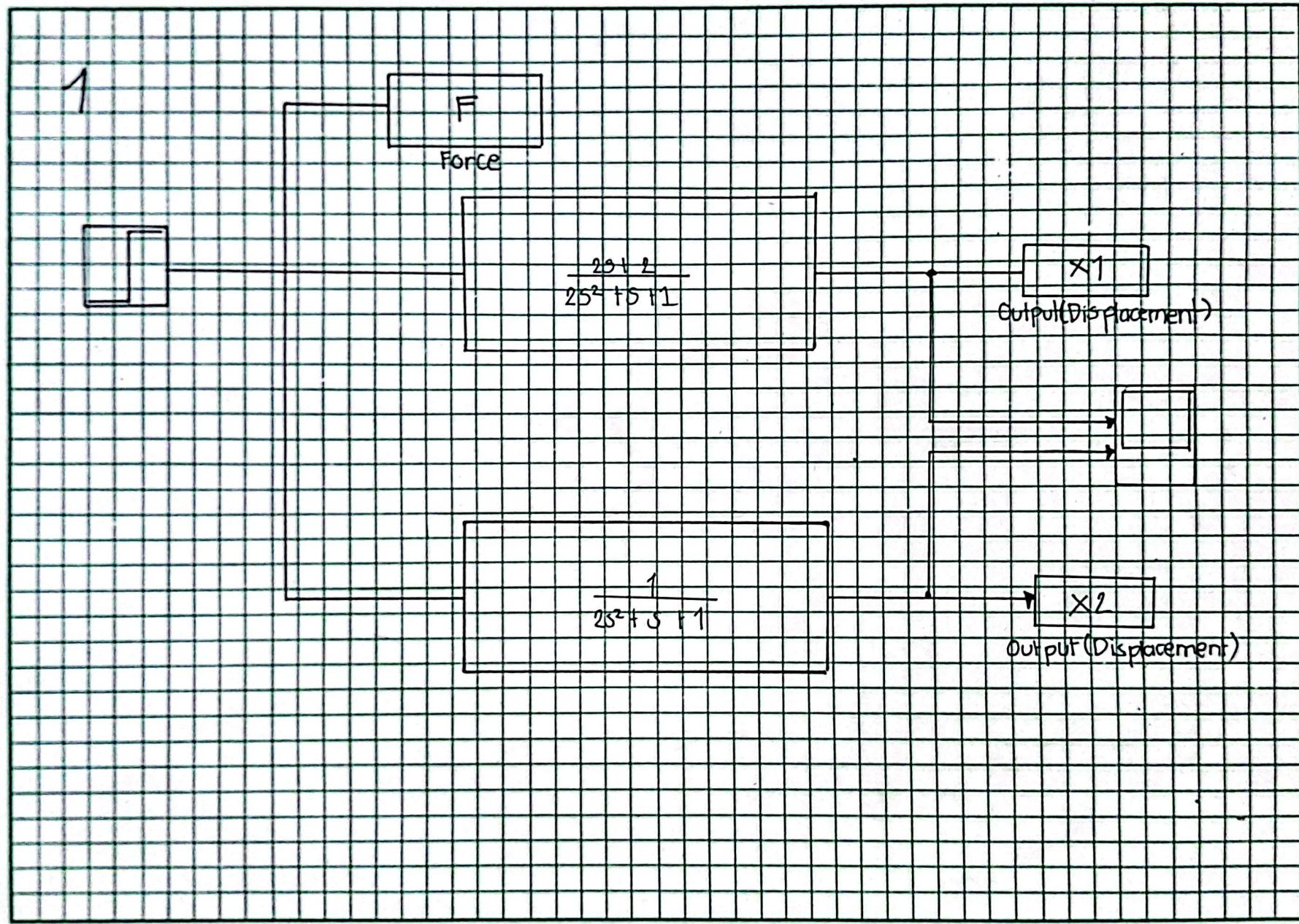

PROBLEM 2

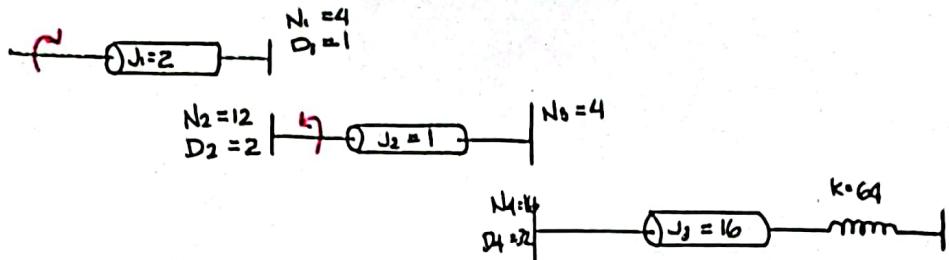

$$R - T(t) = J_e \ddot{\theta}_2 + D_e \dot{\theta}_2 + K_e \theta_2$$

$$R = \frac{N_D}{N_S} = \frac{N_2}{N_1} = \frac{12}{4} = 3$$

$$J_e = \sum \left(\frac{N_D}{N_S} \right)^2 = J_1 \left(\frac{N_2}{N_1} \right)^2 + J_2 \left(\frac{N_2}{N_2} \cdot \frac{N_3}{N_3} \right)^2 + J_3 \left(\frac{N_3}{N_4} \right)^2$$

$$J_e = 2 \left(\frac{12}{4} \right)^2 + 1 \left(\frac{12}{12} \cdot \frac{4}{4} \right)^2 + 16 \left(\frac{4}{16} \right)^2$$

$$J_e = 20$$

$$D_e = \sum \left(\frac{N_D}{N_S} \right)^2 = D_1 \left(\frac{N_2}{N_1} \right)^2 + D_2 \left(\frac{N_2}{N_2} \cdot \frac{N_3}{N_3} \right)^2 + D_3 \left(\frac{N_3}{N_4} \right)^2$$

$$D_e = 1 \left(\frac{12}{4} \right)^2 + 2 \left(\frac{12}{12} \cdot \frac{4}{4} \right)^2 + 32 \left(\frac{4}{16} \right)^2$$

$$D_e = 13$$

$$K_e = \sum \left(\frac{N_D}{N_S} \right)^2 = 64 \left(\frac{4}{16} \right)^2$$


$$K_e = 4$$


$$3T(t) = 20\ddot{\theta}_2 + 13\dot{\theta}_2 + 4\theta_2$$

$$3T(s) = 20s^2\theta_2(s) + 13s\theta_2(s) + 4\theta_2(s)$$

$$3T(s) = \theta_2(s) [20s^2 + 13s + 4]$$

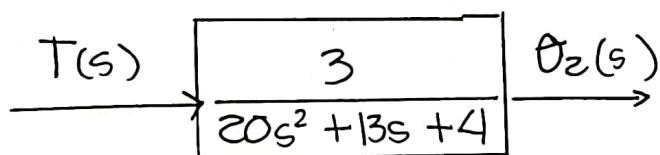
$$\frac{\theta_2(s)}{T(s)} = \frac{3}{20s^2 + 13s + 4}$$



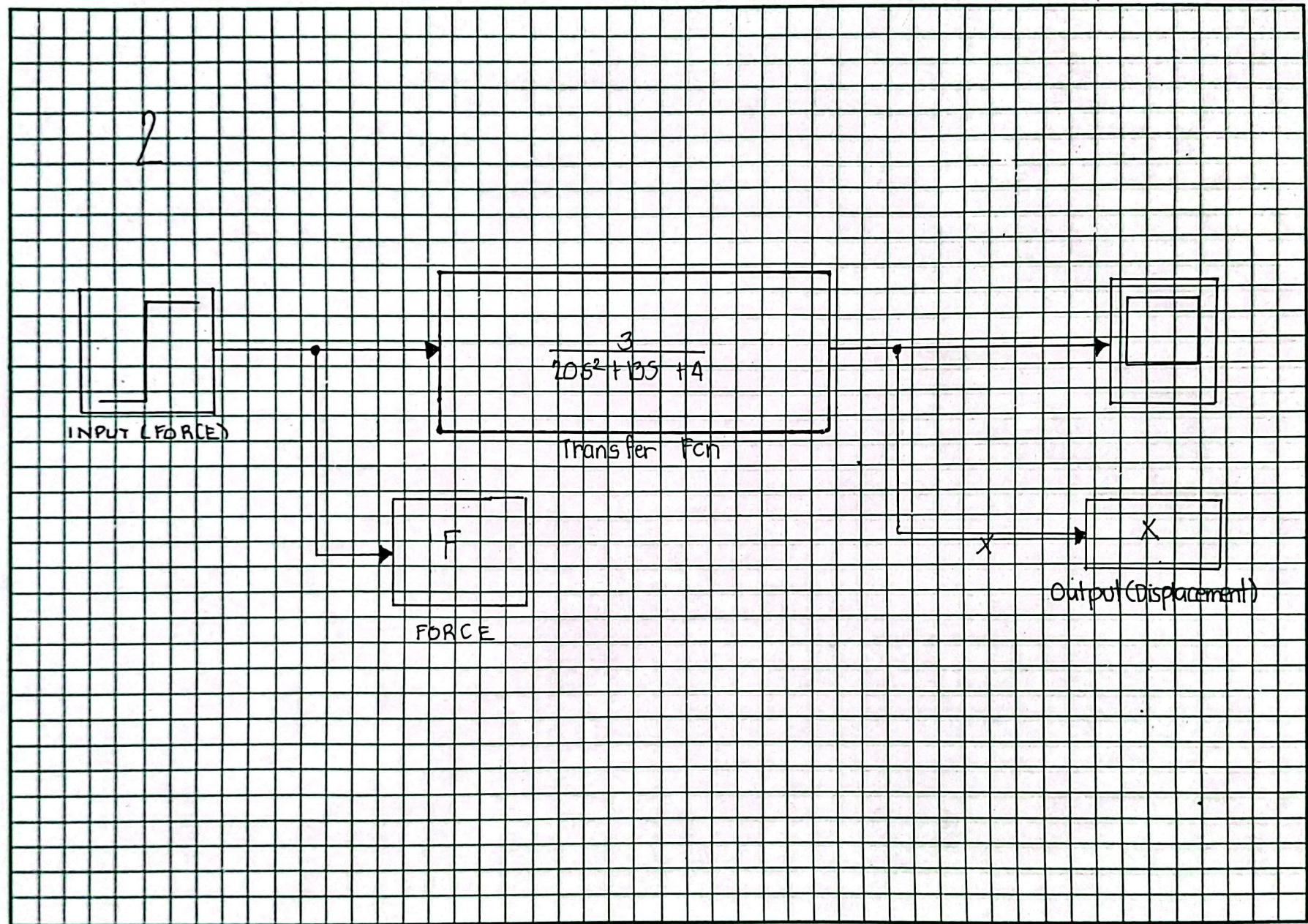

LABORATORY NO.3
GROUP 2

PROBLEM NO. 3 FIG. A

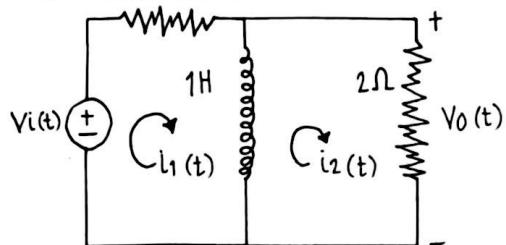

KVL @ loop $i_1(t)$

$$V_i(t) = R_1 i_1(t) + L \frac{di_1(t)}{dt} - L \frac{di_2(t)}{dt}$$

$$\mathcal{L}\{V_i(t) = i_1(t) + \frac{di_1(t)}{dt} - \frac{di_2(t)}{dt}\}$$

$$V_i(s) = I_1(s) + sI_1(s) - sI_2(s)$$

$$V_i(s) = I_1(s)[s+1] - sI_2(s) \quad \textcircled{1}$$

KVL @ loop $i_2(t)$

$$0 = L \frac{di_2(t)}{dt} - R_2 i_2(t) - L \frac{di_1(t)}{dt}$$

$$\mathcal{L}\{0 = \frac{di_2(t)}{dt} + 2i_2(t) - \frac{di_1(t)}{dt}\}$$

$$0 = sI_2(s) + 2I_2(s) - sI_1(s)$$

$$0 = I_2(s)[s+2] - sI_1(s) \quad \textcircled{2}$$

$$I_2(s) = \frac{\begin{bmatrix} s+1 & V_i(s) \\ -s & 0 \end{bmatrix}}{\begin{bmatrix} s+1 & -s \\ -s & s+2 \end{bmatrix}} = \frac{0 - [-sV_i(s)]}{(s+1)(s+2) - s^2}$$

$$I_2(s) = \frac{sV_i(s)}{s^2 + 2s + 1s + 2}$$

$$\frac{I_2(s)}{V_i(s)} = \frac{s}{3s+2}$$

$$VR_2(s) = R_2 I(s)$$

$$VR_2(s) = 2I(s)$$

$$I(s) = \frac{VR_2(s)}{2}$$

$$2 \left[\frac{VR_2(s)}{2V_i(s)} = \frac{s}{3s+2} \right] 2$$

$$\frac{VR_2(s)}{V_i(s)} = \frac{2s}{3s+2}$$

$$\boxed{\frac{2s}{3s+2}}$$

FOR $I_1(s)$:

$$I_1(s) = \frac{\begin{bmatrix} V(s) & -s \\ 0 & s+2 \end{bmatrix}}{\begin{bmatrix} 1+s & -s \\ -s & s+2 \end{bmatrix}} = \frac{V(s)}{s+2s+s^2+2s-s^2}$$

$$I_1(s) = \frac{V(s)[s+2]}{3s+2}$$

$$\frac{I_1(s)}{V(s)} = \frac{s+2}{3s+2}$$

$$\boxed{\frac{s+2}{3s+2}}$$

OR

$$\boxed{\frac{s}{s+2}}$$




CamScanner

Scanned with

CS CamScanner

FIGURE (b)

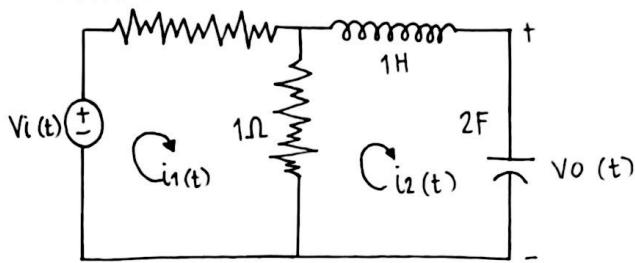

KVL @ loop 1

$$\mathcal{L}\{V(t) = R_1 i_1(t) + R_2 i_1(t) - R_2 i_2(t)\}$$

$$V(s) = R_1 I_1(s) + R_2 I_1(s) - R_2 I_2(s)$$

$$V(s) = 2I_1(s) - I_2(s) \quad ①$$

C A B

KVL @ loop 2

$$0 = R_2 i_2(t) + L \frac{di_2(t)}{dt} + \frac{1}{C} \int i_2(t) dt - R_2 i_1(t)$$

$$\mathcal{L}\{0 = i_2(t) + \frac{di_2(t)}{dt} + \frac{1}{2} \int i_2(t) dt - i_1(t)\}$$

$$0 = I_2(s) + s I_2(s) + \frac{1}{2s} I_2(s) - I_1(s)$$

$$0 = I_2(s) \left[\frac{2s+2s^2+1}{2s} \right] - I_1(s) \quad ②$$

$$I_2(s) = \frac{\begin{bmatrix} 2 & V(s) \\ -1 & 0 \end{bmatrix}}{\begin{bmatrix} 2 & 2s+2s^2+1 \\ -1 & 2s \end{bmatrix}} = \frac{0 - [-V(s)]}{2 \left[\frac{2s+2s^2+1}{2s} \right] - 1}$$

$$I_2(s) = \frac{V(s)}{\frac{4s+4s^2+4}{2s} - 1}$$

$$I_2(s) = \frac{V(s)}{\frac{4s+4s^2+2-2s}{2s}}$$

$$\frac{I_2(s)}{V(s)} = \frac{2s}{4s^2+2s+2}$$

$$\frac{V_C(s)}{I(s)} = \frac{1}{Cs}$$

$$\frac{V_C(s)}{I(s)} = \frac{1}{2s}$$

$$2s V_C(s) = I(s)$$

$$\frac{1}{2s} \left[\frac{2s V_C(s)}{V(s)} = \frac{2s}{4s^2+2s+2} \right] \frac{1}{2s}$$

$$\frac{V_C(s)}{V(s)} = \frac{1}{4s^2+2s+2}$$

$$\frac{V(s)}{V(s)} \rightarrow \boxed{\frac{1}{4s^2+2s+2}} \rightarrow \frac{V_C(s)}{V(s)}$$

FOR $I_1(s)$; FIG. B

$$I_1(s) = \frac{\begin{bmatrix} V(s) & \frac{2s^2+2s+1}{2s} \\ 0 & -1 \end{bmatrix}}{\begin{bmatrix} 2 & -1 \\ -1 & \frac{2s^2+2s+1}{2s} \end{bmatrix}} = \frac{V(s) \left[\frac{2s+2s^2+1}{2s} \right]}{\frac{4s+4s^2+4}{2s} - 1}$$

$$\frac{I_1(s)}{V(s)} = \frac{\frac{2s^2+2s+1}{2s}}{\frac{4s^2+2s+2}{2s}}$$

$$\frac{I_1(s)}{V(s)} = \frac{2s^2+2s+1}{2s} \cdot \frac{2s}{4s^2+2s+2}$$

$$\frac{I_1(s)}{V(s)} = \frac{2s^2+2s+1}{4s^2+2s+2}$$


$$\frac{I_1(s)}{V(s)} = \frac{2s^2+2s+1}{2[2s^2+s+1]}$$

$$\frac{V(s)}{\rightarrow} \boxed{\frac{2s^2+2s+1}{2[2s^2+s+1]}} \xrightarrow{I_1(s)}$$

AND

$$\frac{V(s)}{\rightarrow} \boxed{\frac{2s}{4s^2+2s+2}} \xrightarrow{I_2(s)}$$

3

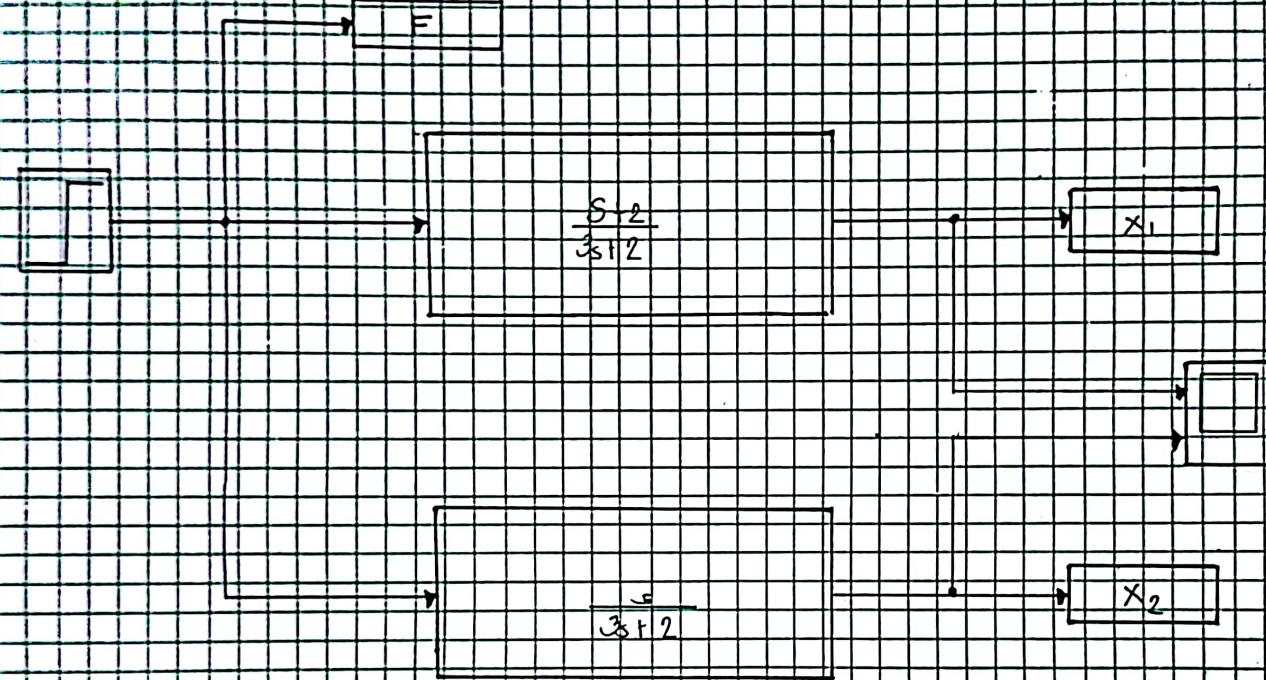

3b

